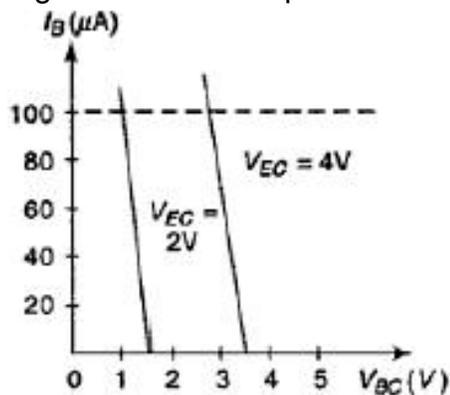


S. E. Computer Engineering (Semester-III)
Choice Based Credit and Grading System (CBCGS)
Electronic Circuits and Communication Fundamentals (CSC304)
Question Bank

- 1) In _____ the operation depends upon the flow of both majority & minority carriers. It is called Bipolar device.
- BJT
 - FET
 - MOSFET
 - SCR

- 2) In Saturation mode of operation of transistor, the emitter-base junction is _____
- Reverse
 - Forward
 - Inverse
 - Counter

- 3) Figure shows the input characteristics of common _____ configuration




- Base
 - Emitter
 - Collector
 - Aerial
- 4) BJT based Crystal Oscillator provides high _____
- Stability
 - Impedance
 - Capacitance
 - Oscillations

- 5) The power gain in single stage amplifier is achieved by _____
 - a) Darlington Transistor
 - b) Pair Transistor
 - c) Quad Transistor
 - d) Single Transistor

- 6) Flat frequency response is achieved by _____ coupling
 - a) RC
 - b) LC
 - c) RL
 - d) Transformer

- 7) Op-amp is said to be ideal if _____
 - a) Open Loop Voltage Gain is Zero
 - b) Input Impedance is Zero
 - c) Output Impedance is Zero
 - d) Bandwidth is Zero

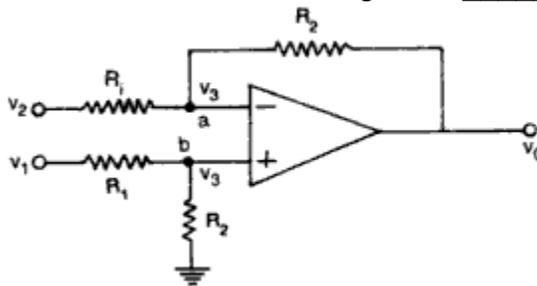- 8) The circuit shown in the figure is _____




- a) An Inverting Amplifier
 - b) A Non Inverting Amplifier
 - c) A Differential Amplifier
 - d) A Summing Amplifier

- 9) To achieve high value of Common Mode Rejection Ratio (CMRR) for ideal Op-amp, the common mode gain should be _____
 - a) Large
 - b) Small
 - c) Zero
 - d) Non-zero

- 10) In an inverting amplifier using op-amp, if input resistor is replaced by capacitor then the circuit is called as _____
 - a) Infinite gain amplifier
 - b) Unity gain amplifier
 - c) Integrator amplifier

d) Differentiator amplifier

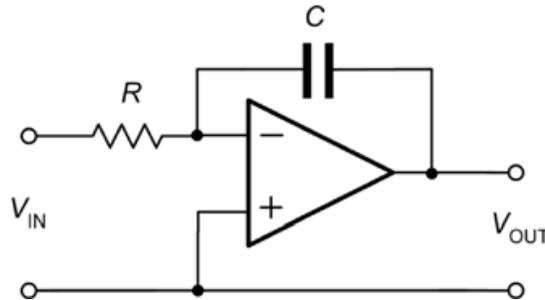11) The circuit shown in the figure is _____



- a) Voltage follower
- b) Differentiator
- c) An integrator
- d) Comparator

12) Slew-rate of ideal Op-amp is _____

- a) Infinite
- b) Zero
- c) Cannot measured
- d) Can estimate

13) A _____ converts the electrical signal back to a form understandable by humans.

- a) Transmitter
- b) Receiver
- c) Channel
- d) Noise

14) In _____, the amount of phase shift of a constant-frequency carrier is varied in accordance with a modulating signal.

- a) Amplitude Modulation (AM)
- b) Frequency Modulation (FM)
- c) Phase Modulation (PM)
- d) Digital Modulation (DM)


15) AM generates _____ number of sidebands

- a) 1
- b) 2
- c) 3
- d) More than 3

16) In FM, the amount of change in carrier frequency produced by the modulating signal is known as the _____

- a) Frequency deviation
- b) Modulating factor
- c) Coefficient of modulation
- d) The degree of modulation

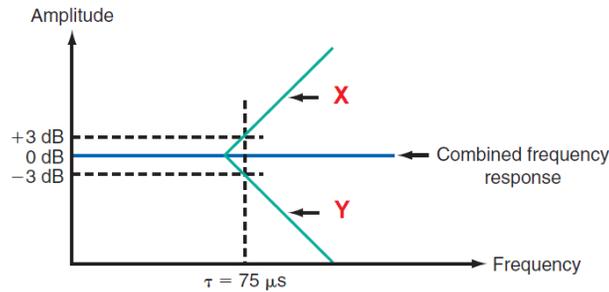17) Frequency response marked with 'X' is a response of _____



- a) Pre-emphasis Circuit
- b) De-emphasis circuit
- c) Modulator circuit
- d) De-modulator circuit


18) RF amplifier in a superhetrodyne receiver is also called a _____

- a) Low-noise amplifier (LNA)
- b) High noise amplifier (HNA)
- c) High power amplifier (HPA)
- d) Low power amplifier (LPA)

19) When Sampling frequency is equal to twice of the incoming signal frequency is called _____

- a) Sampling Theorem
- b) Sampling Technique
- c) Nyquist Rate
- d) Interpolation

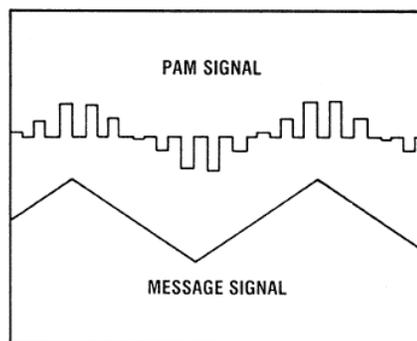20) The PAM signal shown in the figure is a _____



- a) Flat-top sampling

- b) Natural sampling
 - c) Pulse Sampling
 - d) Width Sampling
- 21) PPM has a similar noise performance as _____
- a) AM
 - b) FM
 - c) PM
 - d) DM
- 22) The fact that information can be measured, was one of the earliest and most important results of _____ theory
- a) Information
 - b) Sampling
 - c) Communication
 - d) Digital
- 23) According to Shannon, the capacity of a link is measured in _____
- a) Bits per second (bps)
 - b) Decibels (dB)
 - c) Watt (W)
 - d) Joule (J)
- 24) As per Shannon, _____ can be defined axiomatically, as a function satisfying several natural conditions.
- a) Entropy
 - b) Joint entropy
 - c) Conditional entropy
 - d) Un-Conditional entropy
- 25) According to Shannon's Theorem, if the information rate is _____ the channel capacity then transmission may be accomplished without error in the presence of noise.
- a) Greater
 - b) Less
 - c) Equal
 - d) Not equal